

# Basic IIR Digital Filter Structures

- The causal IIR digital filters we are concerned with in this course are characterized by a real rational transfer function of  $z^{-1}$  or, equivalently by a constant real coefficient difference equation
- From the difference equation representation, it can be seen that the realization of the causal IIR digital filters requires some form of feedback

# Basic IIR Digital Filter Structures

- An  $N$ -th order IIR digital transfer function is characterized by  $2N+1$  unique coefficients, and in general, requires  $2N+1$  multipliers and  $2N$  two-input adders for implementation
- **Direct form IIR filters:** Filter structures in which the multiplier coefficients are precisely the coefficients of the transfer function


# Direct Form IIR Digital Filter Structures

- Consider for simplicity a 3rd-order IIR filter with a transfer function

$$H(z) = \frac{P(z)}{D(z)} = \frac{p_0 + p_1z^{-1} + p_2z^{-2} + p_3z^{-3}}{1 + d_1z^{-1} + d_2z^{-2} + d_3z^{-3}}$$

- We can implement  $H(z)$  as a cascade of two filter sections as shown on the next slide
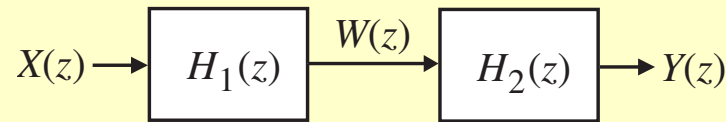
# Direct Form IIR Digital Filter Structures



where


$$H_1(z) = \frac{W(z)}{X(z)} = P(z) = p_0 + p_1 z^{-1} + p_2 z^{-2} + p_3 z^{-3}$$

$$H_2(z) = \frac{Y(z)}{W(z)} = \frac{1}{D(z)} = \frac{1}{1 + d_1 z^{-1} + d_2 z^{-2} + d_3 z^{-3}}$$
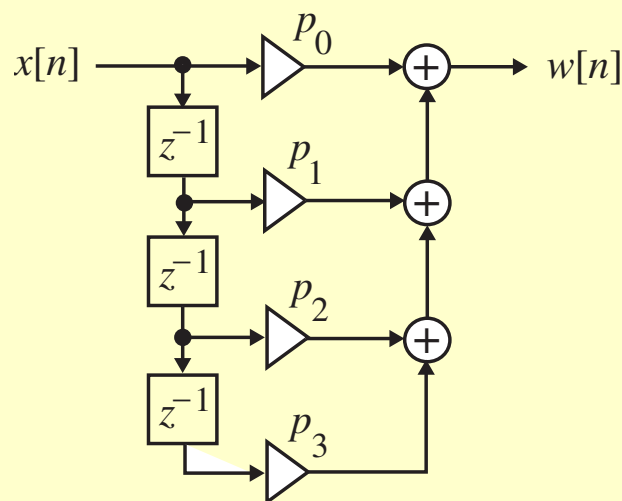
# Direct Form IIR Digital Filter Structures

- The filter section  $H_1(z)$  can be seen to be an FIR filter and can be realized as shown below

$$w[n] = p_0x[n] + p_1x[n-1] + p_2x[n-2] + p_3x[n-3]$$




# Direct Form IIR Digital Filter Structures

- The time-domain representation of  $H_2(z)$  is given by


$$y[n] = w[n] - d_1 y[n-1] - d_2 y[n-2] - d_3 y[n-3]$$

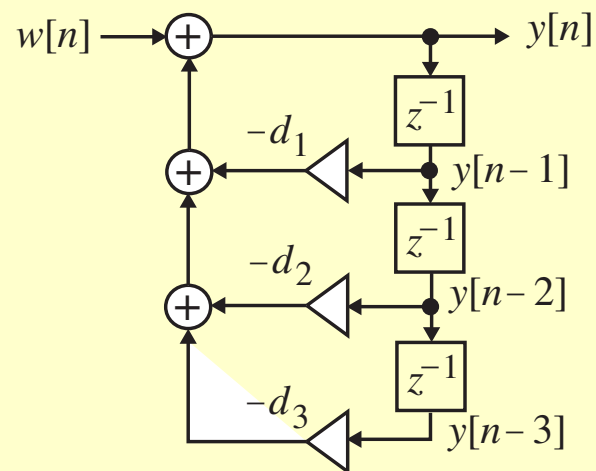Realization of  $H_2(z)$  follows from the above equation and is shown on the right



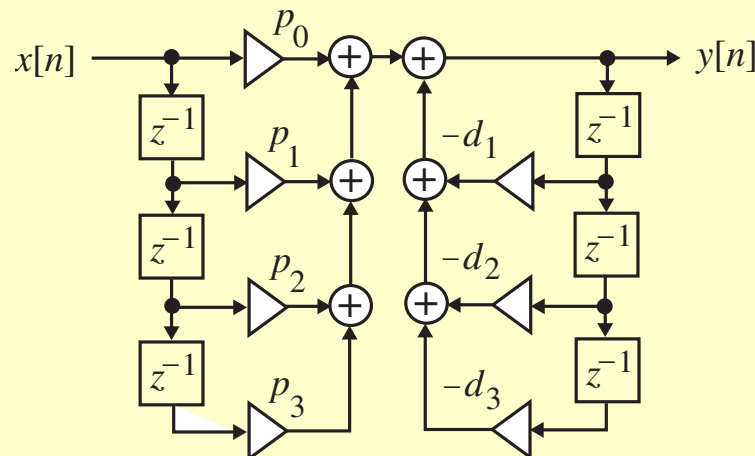
# Direct Form IIR Digital Filter Structures

- A cascade of the two structures realizing  $H_1(z)$  and  $H_2(z)$  leads to the realization of  $H(z)$  shown below and is known as the **direct form I** structure


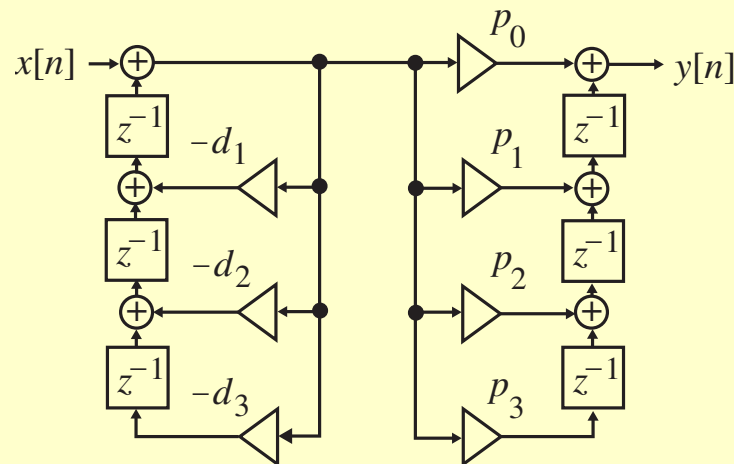
# Direct Form IIR Digital Filter Structures



- Note: The direct form I structure is noncanonic as it employs 6 delays to realize a 3rd-order transfer function
- A transpose of the direct form I structure is shown on the right and is called the direct form  $I_t$  structure





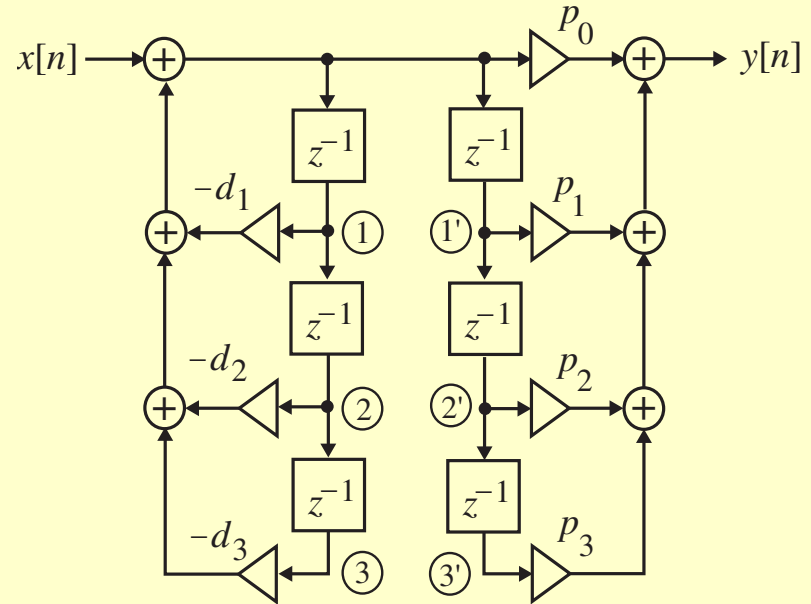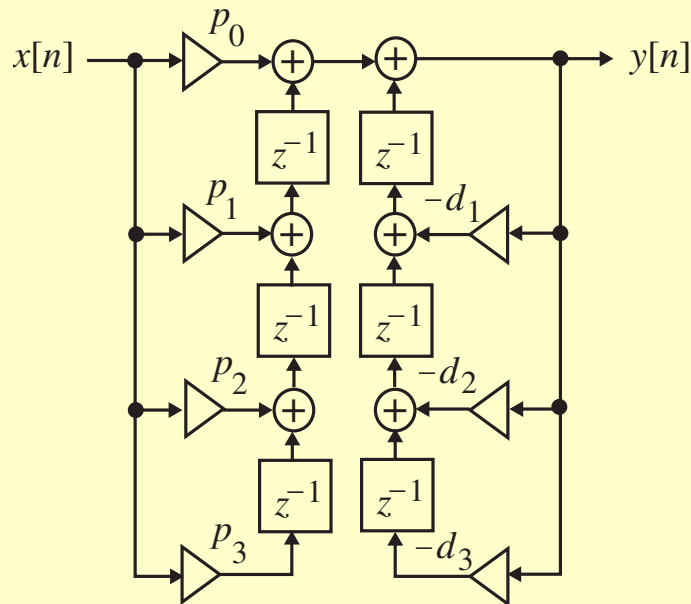
# Direct Form IIR Digital Filter Structures

- Various other noncanonic direct form structures can be derived by simple block diagram manipulations as shown below


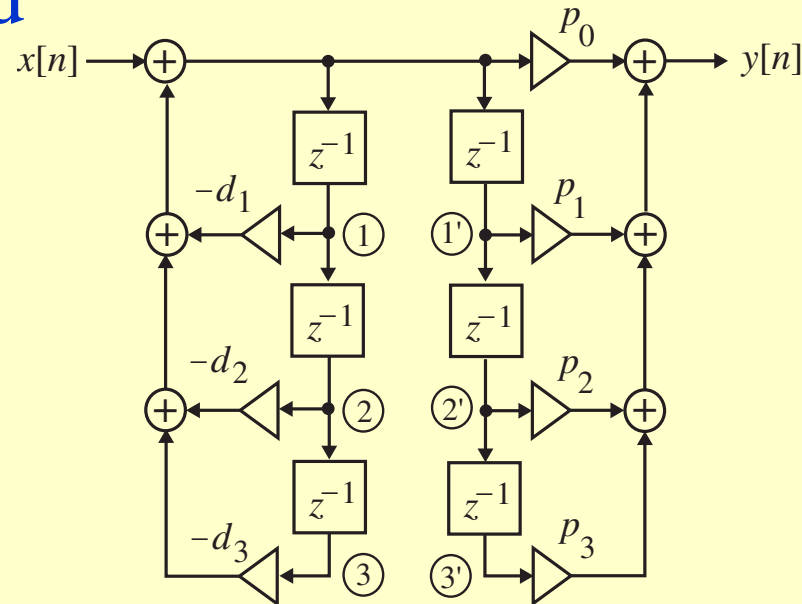
# Direct Form IIR Digital Filter Structures


- Observe in the direct form structure shown below, the signal variable at nodes ① and ①' are the same, and hence the two top delays can be shared



# Direct Form IIR Digital Filter Structures

- Likewise, the signal variables at nodes ② and ②' are the same, permitting the sharing of the middle two delays
- Following the same argument, the bottom two delays can be shared
- Sharing of all delays reduces the total number of delays to 3 resulting in a canonic realization shown on the next slide along with its transpose structure
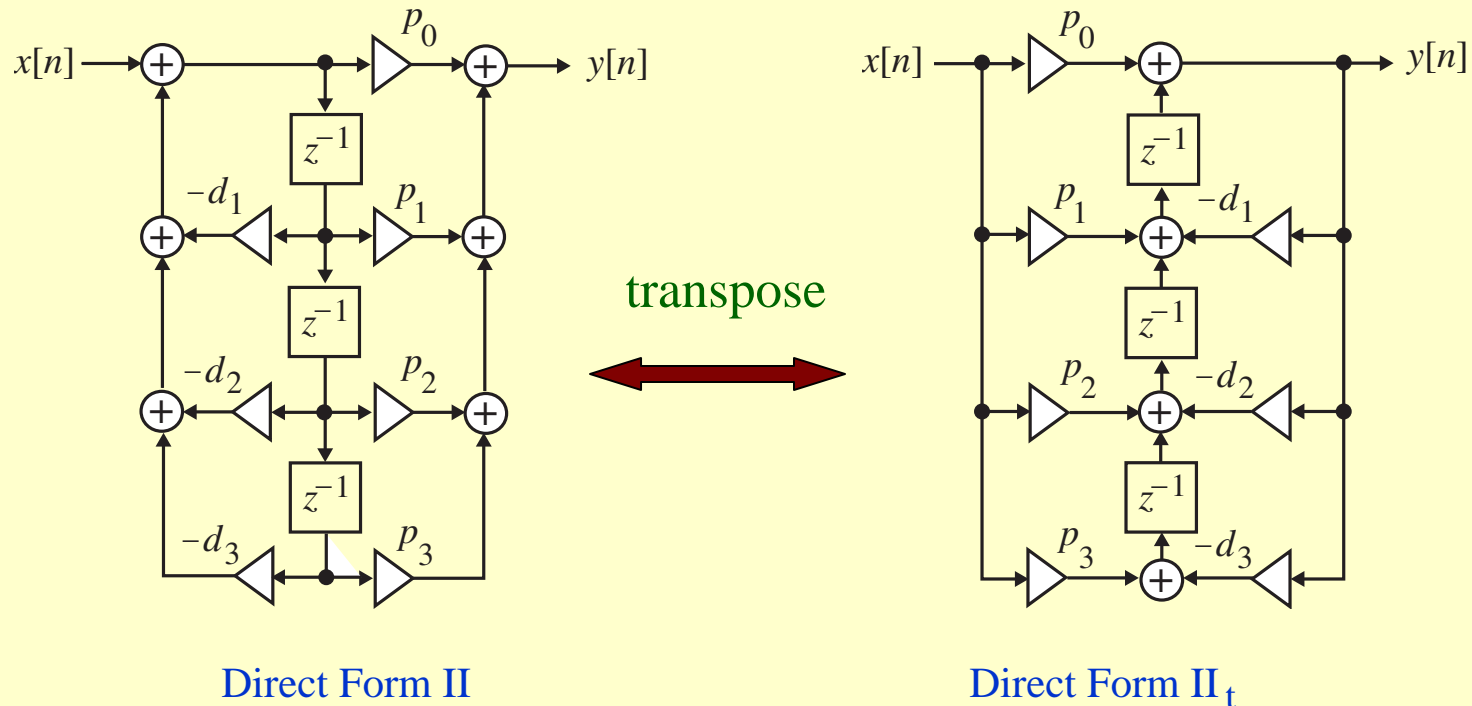
# Direct Form IIR Digital Filter Structures



- Direct form realizations of an  $N$ -th order IIR transfer function should be evident


# Cascade Form IIR Digital Filter Structures

- By expressing the numerator and the denominator polynomials of the transfer function as a product of polynomials of lower degree, a digital filter can be realized as a cascade of low-order filter sections
- Consider, for example,  $H(z) = P(z)/D(z)$  expressed as

$$H(z) = \frac{P(z)}{D(z)} = \frac{P_1(z)P_2(z)P_3(z)}{D_1(z)D_2(z)D_3(z)}$$


# Cascade Form IIR Digital Filter Structures

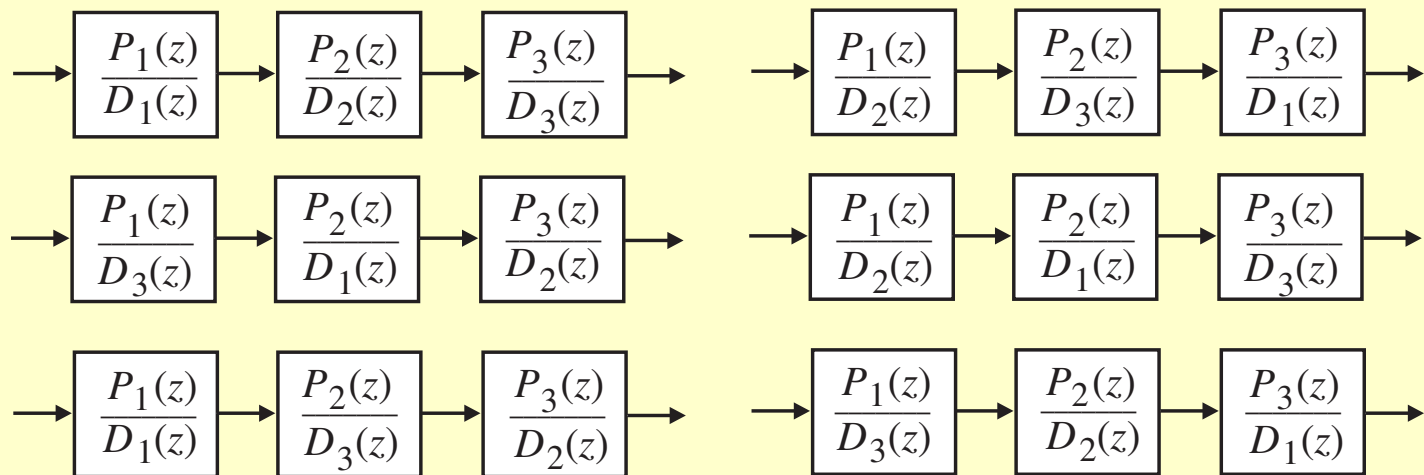- Examples of cascade realizations obtained by different pole-zero pairings are shown below



# Cascade Form IIR Digital Filter Structures

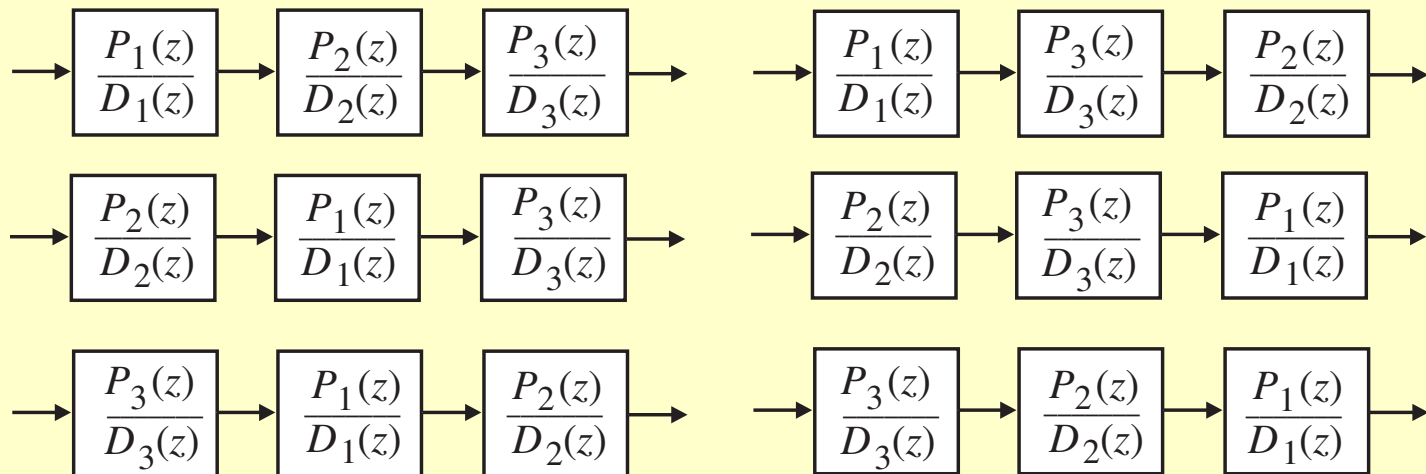- Examples of cascade realizations obtained by different ordering of sections are shown below



# Cascade Form IIR Digital Filter Structures

- There are altogether a total of 36 different cascade realizations of

$$H(z) = \frac{P_1(z)P_2(z)P_2(z)}{D_1(z)D_2(z)D_3(z)}$$

based on pole-zero-pairings and ordering

- Due to finite wordlength effects, each such cascade realization behaves differently from others



# Cascade Form IIR Digital Filter Structures

- Usually, the polynomials are factored into a product of 1st-order and 2nd-order polynomials:

$$H(z) = p_0 \prod_k \left( \frac{1 + \beta_{1k} z^{-1} + \beta_{2k} z^{-2}}{1 + \alpha_{1k} z^{-1} + \alpha_{2k} z^{-2}} \right)$$

- In the above, for a first-order factor


$$\alpha_{2k} = \beta_{2k} = 0$$

# Cascade Form IIR Digital Filter Structures

- Consider the 3rd-order transfer function

$$H(z) = p_0 \left( \frac{1 + \beta_{11}z^{-1}}{1 + \alpha_{11}z^{-1}} \right) \left( \frac{1 + \beta_{12}z^{-1} + \beta_{22}z^{-2}}{1 + \alpha_{12}z^{-1} + \alpha_{22}z^{-2}} \right)$$

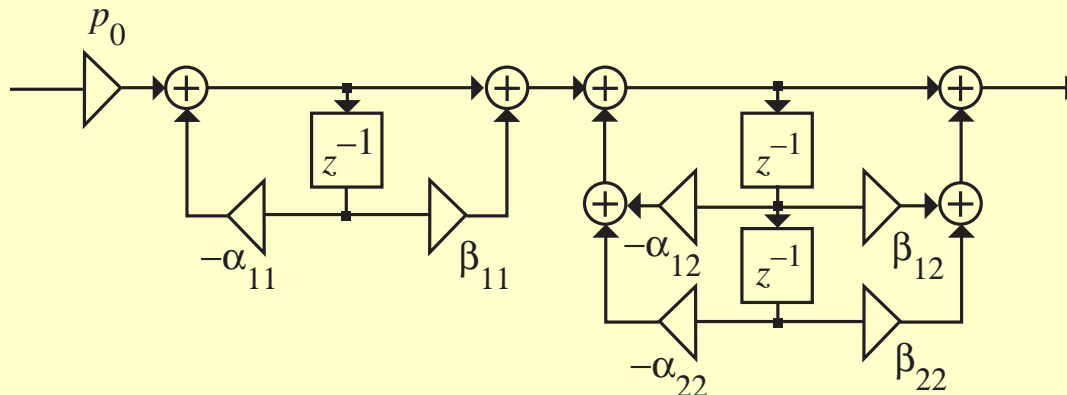- One possible realization is shown below




# Cascade Form IIR Digital Filter Structures

- Example - Direct form II and cascade form realizations of


$$H(z) = \frac{0.44z^{-1} + 0.362z^{-2} + 0.02z^{-3}}{1 + 0.4z^{-1} + 0.18z^{-2} - 0.2z^{-3}}$$
$$= \left( \frac{0.44 + 0.362z^{-1} + 0.02z^{-2}}{1 + 0.8z^{-1} + 0.5z^{-2}} \right) \left( \frac{z^{-1}}{1 - 0.4z^{-1}} \right)$$

are shown on the next slide
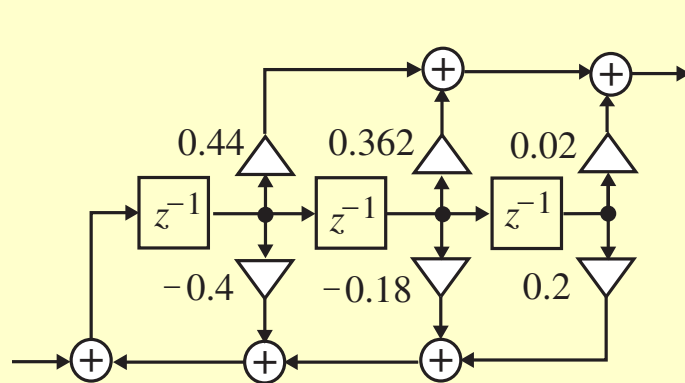
# Cascade Form IIR Digital Filter Structures



Direct form II

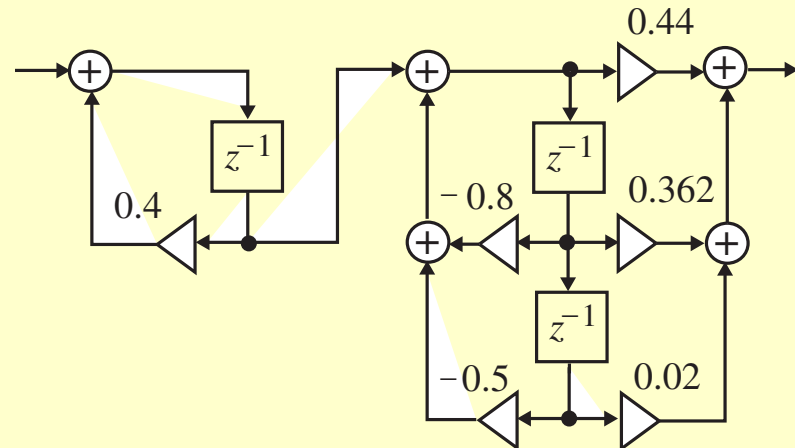

Cascade form

# Parallel Form IIR Digital Filter Structures

- A partial-fraction expansion of the transfer function in  $z^{-1}$  leads to the **parallel form I** structure
- Assuming simple poles, the transfer function  $H(z)$  can be expressed as

$$H(z) = \gamma_0 + \sum_k \left( \frac{\gamma_{0k} + \gamma_{1k} z^{-1}}{1 + \alpha_{1k} z^{-1} + \alpha_{2k} z^{-2}} \right)$$

- In the above for a real pole  $\alpha_{2k} = \gamma_{1k} = 0$

# Parallel Form IIR Digital Filter Structures


- A direct partial-fraction expansion of the transfer function in  $z$  leads to the **parallel form II** structure
- Assuming simple poles, the transfer function  $H(z)$  can be expressed as

$$H(z) = \delta_0 + \sum_k \left( \frac{\delta_{1k}z^{-1} + \delta_{2k}z^{-2}}{1 + \alpha_{1k}z^{-1} + \alpha_{2k}z^{-2}} \right)$$


- In the above for a real pole  $\alpha_{2k} = \delta_{2k} = 0$
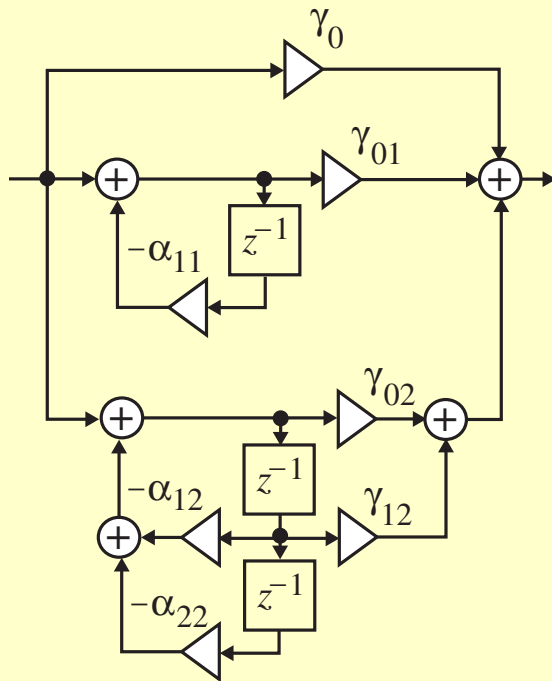
# Parallel Form IIR Digital Filter Structures

- The two basic parallel realizations of a 3rd-order IIR transfer function are shown below



Parallel form I

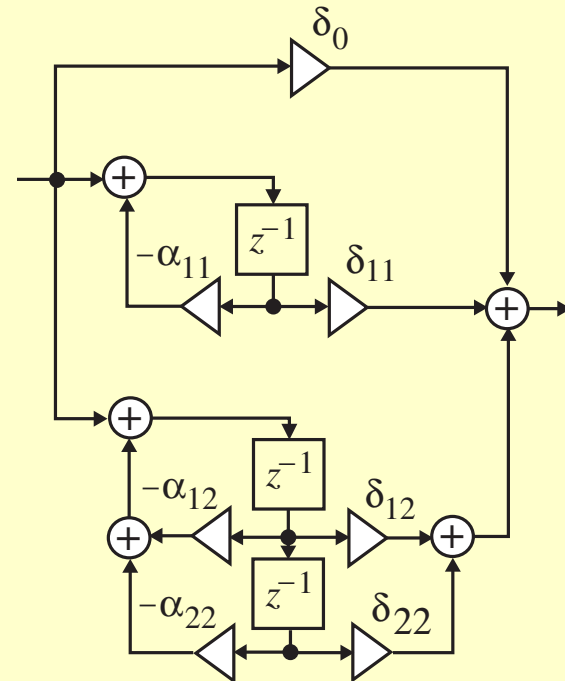

Parallel form II

# Parallel Form IIR Digital Filter Structures

- Example - A partial-fraction expansion of

$$H(z) = \frac{0.44z^{-1} + 0.362z^{-2} + 0.02z^{-3}}{1 + 0.4z^{-1} + 0.18z^{-2} - 0.2z^{-3}}$$


in  $z^{-1}$  yields

$$H(z) = -0.1 + \frac{0.6}{1 - 0.4z^{-1}} + \frac{-0.5 - 0.2z^{-1}}{1 + 0.8z^{-1} + 0.5z^{-2}}$$


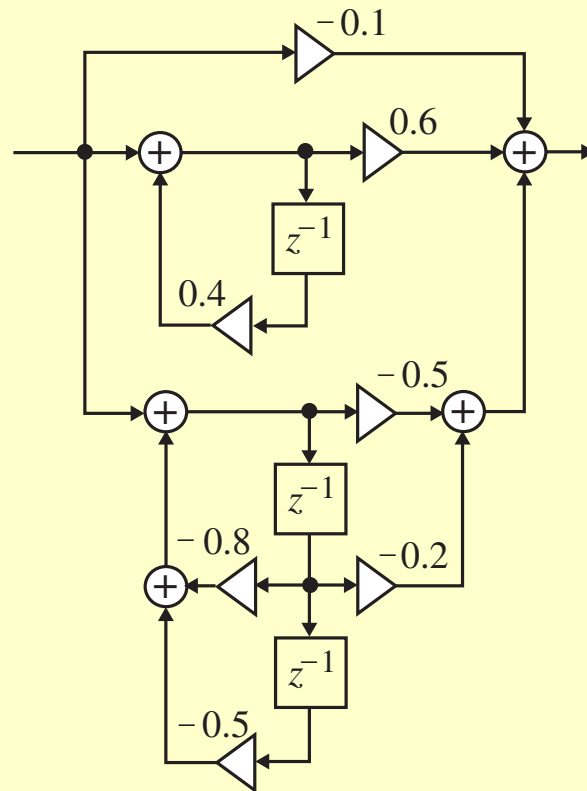
# Parallel Form IIR Digital Filter Structures

- The corresponding parallel form I realization is shown below




# Parallel Form IIR Digital Filter Structures

- Likewise, a partial-fraction expansion of  $H(z)$  in  $z$  yields

$$H(z) = \frac{0.24z^{-1}}{1-0.4z^{-1}} + \frac{0.2z^{-1} + 0.25z^{-2}}{1+0.8z^{-1}+0.5z^{-2}}$$

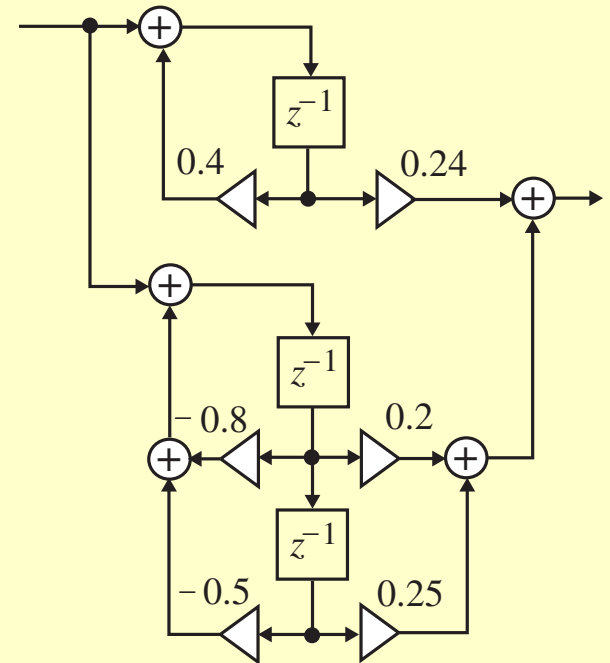- The corresponding parallel form II realization is shown on the right



# Realization Using MATLAB

- The cascade form requires the factorization of the transfer function which can be developed using the M-file `zp2sos`
- The statement `sos = zp2sos(z, p, k)` generates a matrix `sos` containing the coefficients of each 2nd-order section of the equivalent transfer function  $H(z)$  determined from its pole-zero form

# Realization Using MATLAB

- `sos` is an  $L \times 6$  matrix of the form

$$\text{sos} = \begin{bmatrix} p_{01} & p_{11} & p_{21} & d_{01} & d_{11} & d_{21} \\ p_{02} & p_{12} & p_{22} & d_{02} & d_{12} & d_{22} \\ \vdots & \vdots & \vdots & \vdots & \vdots & \vdots \\ p_{0L} & p_{1L} & p_{2L} & d_{0L} & d_{1L} & d_{2L} \end{bmatrix}$$

whose  $i$ -th row contains the coefficients  $\{p_{i\ell}\}$  and  $\{d_{i\ell}\}$ , of the the numerator and denominator polynomials of the  $i$ -th 2nd-order section

# Realization Using MATLAB

- $L$  denotes the number of sections
- The form of the overall transfer function is given by

$$H(z) = \prod_{i=1}^L H_i(z) = \prod_{i=1}^L \frac{p_{0i} + p_{1i}z^{-1} + p_{2i}z^{-2}}{d_{0i} + d_{1i}z^{-1} + d_{2i}z^{-2}}$$

- Program 6\_1 can be used to factorize an FIR and an IIR transfer function

# Realization Using MATLAB

- **Note:** An FIR transfer function can be treated as an IIR transfer function with a constant numerator of unity and a denominator which is the polynomial describing the FIR transfer function

# Realization Using MATLAB

- Parallel forms I and II can be developed using the functions `residuez` and `residue`, respectively
- Program 6\_2 uses these two functions